

Name \_\_\_\_\_

## CSE222 Computer Architecture

### Quiz 02

1. Design a circuit that has a 3-bit binary input and a single output (Y) as specified in followings:
  - $Y = 0$  if the inputs is less than  $(5)_{10}$
  - $Y = 1$  if the inputs is greater than or equal to  $(5)_{10}$
- (a) Specify the function in truth table
- (b) Describe the function in Boolean expression in SOP form, then simplify this Boolean equation, build the circuit using logical gates
- (c) Draw the Logical Diagrams in other functional circuits:
  - (c1) Build the circuit using 4:1 multiplexer
  - (c2) Build the circuit using 2:1 multiplexer(s)
  - (c3) Build the circuit using 3:8 decoder