

## Final Project Part I

1. To convert a 4-bit signed/magnitude binary number to two's complement you would have 4 inputs: A, B, C, D to represent the signed binary number. A is the msb and D is the lsb. For the output, you would have 4 outputs: Y0, Y1, Y2, Y3 to represent two's complement. Y0 is the msb and Y3 is the lsb. First take A and connect it to an AND gate with a constant high voltage. We do this to check if the signed binary number is negative. If A\*1 is 0 then we return A = Y0, B = Y1, C = Y2, and D = Y3 because a positive number in signed/magnitude is the same in two's complement format. If A\*1 is 1,then the signed binary number is negative, so we negate B, C, and D. Then we can use XOR and AND gates to build half adders and full adders to add 1 to the lsb and use it's cout to add C, then repeat for B and A. When we add A and B's cout, we discard A's cout since were only working in a 4 bit system. Finally, you have your signed binary number in two's complement.


2.	ABCD	Yo	Υ,	Y2	Y3	3
	0000	0	ο`	0	٥	
	0001	٥	0	0	l	Yo = A(B+C+D)
	0010	0	0	1	0	
	0011	0	0	1	1	V 70 000 10/0 00
	0100	0	ι .	٥	0	Y = AB + BCD + AB (C+D)
	0101	0	1	0	1	
	0110	C	t	١	0	\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\\
	0111	٥	1	1	ι	Y2= ACD+ AC+ CD
	1000	٥	٥	٥	0	
	1001	ı	ı	ı	l	. /
	1010	1	l	١	0	$Y_3 = D$
	1011	ı	1	0	ı	
	1100	ı	١	٥	0	
	1101	1	0	ı	l	
	1110	L.	٥	1	٥	
	till	1	0	0	1	

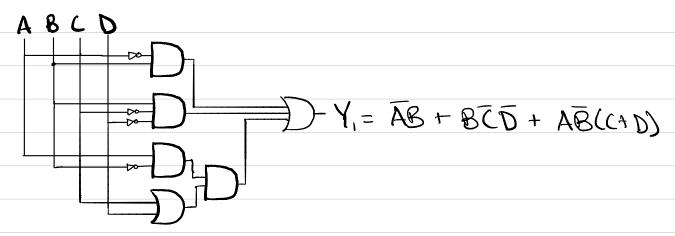

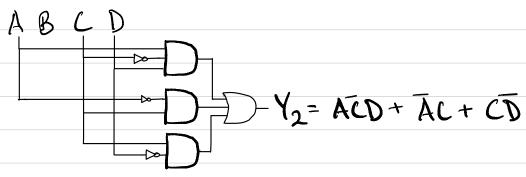



$$D-Y_3=D$$

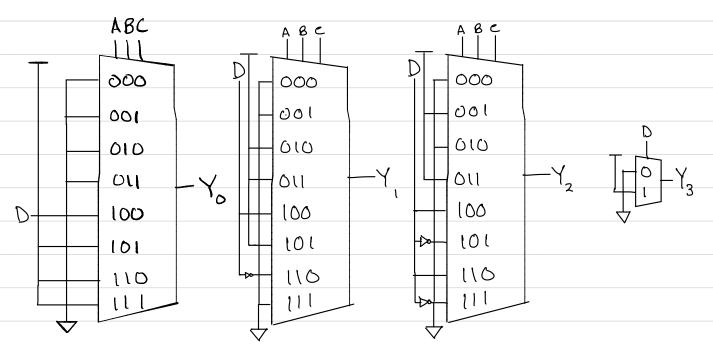

## Final Project Part II

- 2. MIPS Program implemented in Campos\_CSE222\_Final\_Project.asm file.