



## CSE222 Computer Architecture Homework Set 06

### (Review)

1. Logic Gates & Circuits
2. Circuits: Combinational Circuits, Sequential Circuits
3. Notations: Truth table, Boolean equations, Logic Diagram
4. Boolean equations: literals, complement, minterm, maxterm, SOP form, POS form
5. Boolean algebra & Boolean equation simplification
6. K-Map

### (Exercise)

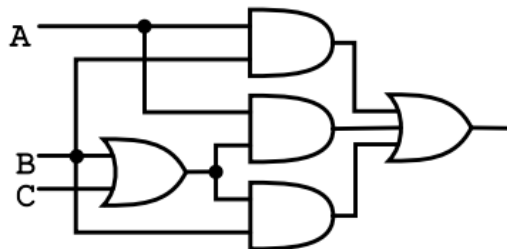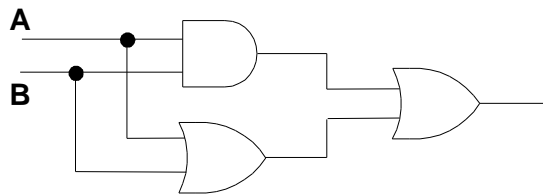1. Given below Boolean equations, draw truth tables and circuit diagrams
  - a.  $F = (A + B)(\bar{B} + C)$
  - b.  $F = \overline{AB} + BC$
  - c.  $F = C + B(A + \bar{C})$
2. Simplify the following Boolean Equations, and draw circuit diagrams:
  - a.  $F = \bar{A}B + \bar{A}(B+C) + B(\bar{B} + C)$
  - b.  $F = (\bar{A}\bar{B} (C+BD) + \bar{A}\bar{B}) C$
  - c.  $F = \bar{A}BC + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + A\bar{B}C + ABC$
3. Describe the behavior of the following circuits with truth table and Boolean equations. Simply the Boolean equations if possible, and draw the simplified diagrams:



4. For truth tables as shown in below:

- Write Boolean equations in SOP (Sum-Of-Product) form, and draw diagram
- Write Boolean equations in POS (Product-Of-Sum) forms, and draw diagram
- Simplify Boolean equations, draw the simplified logic diagrams

A	B	C	F	minterm	maxterm
0	0	0	1		
0	0	1	1		
0	1	0	0		
0	1	1	0		
1	0	0	0		
1	0	1	0		
1	1	0	1		
1	1	1	1		

A	B	C	D	F	minterm	maxterm
0	0	0	0	1		
0	0	0	1	1		
0	0	1	0	1		
0	0	1	1	1		
0	1	0	0	0		
0	1	0	1	0		
0	1	1	0	0		
0	1	1	1	0		
1	0	0	0	1		
1	0	0	1	0		
1	0	1	0	1		
1	0	1	1	0		
1	1	0	0	0		
1	1	0	1	0		
1	1	1	0	1		
1	1	1	1	0		

5. Use K-Map to simplify the following Boolean equations, draw circuit diagrams after simplification

(a)  $Y = \overline{A}BC + \overline{A}\overline{B}\overline{C}$

(b)  $Y = \overline{A}\overline{B}\overline{C} + A\overline{B}$

(c)  $Y = ABC\overline{D} + \overline{A}\overline{B}\overline{C}\overline{D} + (\overline{A} + \overline{B} + \overline{C} + \overline{D})$